



North South University

Department of Electrical & Computer Engineering

LAB REPORT

Spring 2021

Course Code : EEE 111

Course Title: Analog Electronics - I

Section: 7

Experiment Number: 02

Experiment Name:

Diode Rectifier Circuits

Experiment Date: 23 / 03 / 2021

Date of Submission: 06 / 04 / 2021

Course Instructor: Syeda Sarita Hassan

Submitted To: Fatema Zahra

Name of experiment:

Diode Rectifier Circuits

Objective:

Study of different diode rectifier circuits.

Equipments:

- ① P-n junction diode - 1N4007 - 4 piece.
- ② Resistor - $10k\Omega$ - 1 piece.
- ③ Capacitor - $0.22\mu F$, $10\mu F$ - 1 piece each.
- ④ Signal generator - 1 piece.
- ⑤ Trainer Board - 1 unit.
- ⑥ Oscilloscope - 1 unit.
- ⑦ Digital Multimeter - 1 unit.
- ⑧ Chords and wire - as required.

(p.t.o)



Theory:

Sometimes it might be necessary to convert an AC (Alternating Current) signal to a DC (Direct Current). This conversion is done by a rectifier. From lab one we already know that a diode only allows current flow if it is in forward biasing. But the output of the diode can be changed depending on the alternating voltage. There are two types of diode rectifiers:

- i) Half-wave rectifier
- ii) Full wave rectifier

Full wave rectifier can be of another type. which is Full-wave bridge rectifier. In the bridge rectifier four diodes are connected in a bridge formation.

Circuit Diagram:

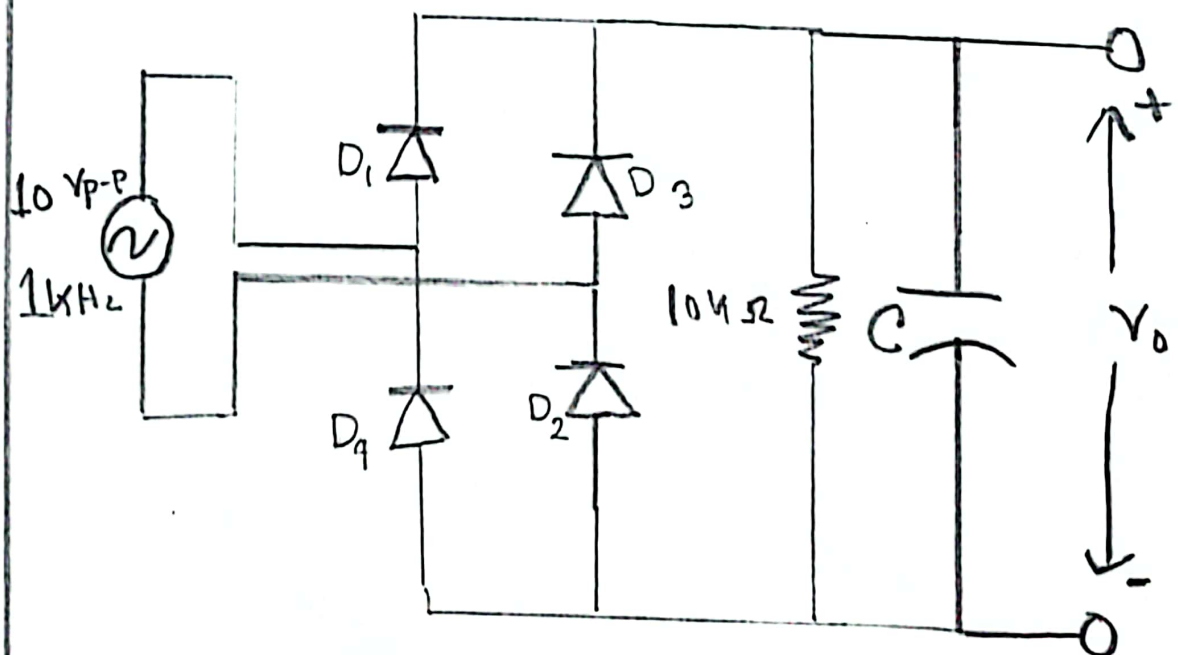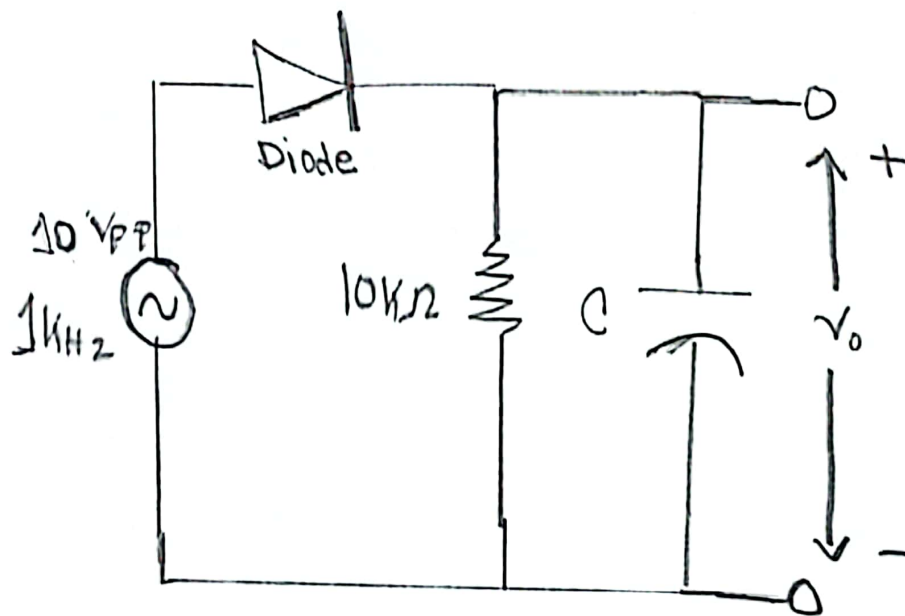

Question & Answer :

① Answer's From working procedure 5-10.

Ans:

⑤ Ans: When we change frequency from 10 kHz to 100 Hz, we can observe that the output line is much straighter on 10 kHz than on 100 Hz.

⑥ Ans: without capacitor the circuit will generate a rippled output in DC.

⑦ Ans: The input voltage is a full wave form but the output voltage is a half wave form.

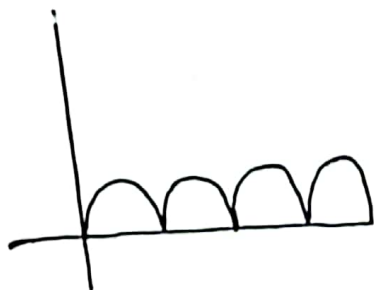


Fig: output


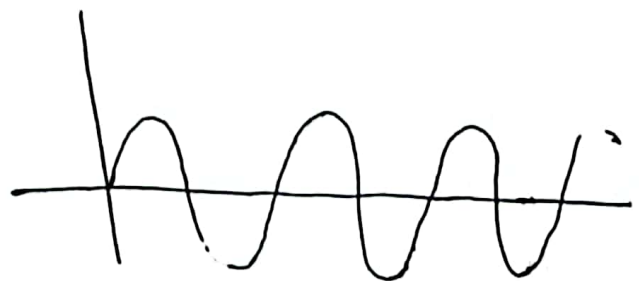
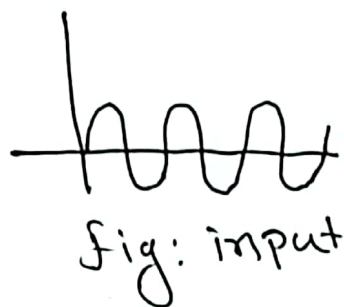


Fig: input



⑧ Ans:

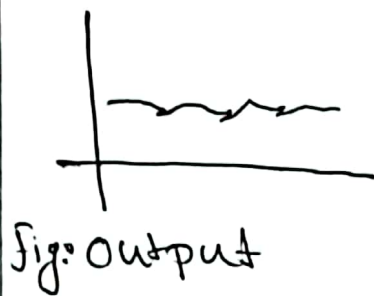After connecting $0.22\mu F$ the output wave got ~~same~~ smoother and the input wave was same as without capacitor.



⑨ Ans:

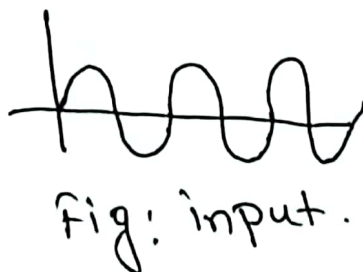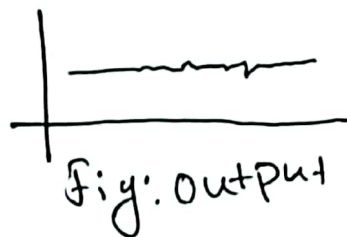After connecting $10\mu F$ the output wave got really smoother almost like a straight line. the input was the same.



Question ⑩ and ⑨ are same.

② Ans: The wave forms are added to the pdf. It's the multism ~~io~~ graphs.

③ Ans: By increasing input frequency the output frequency wave lengths tend to much shorter (like ripple). But decreasing gives long waves. so we can say

$$f_i \propto \frac{1}{f_o} \cdot \text{~~and~~}$$

④ Ans: Capacitor can reduce ripple wave forms and make the output DC signal much stable and smoother. Capacitor does this by charging and discharging.


A higher capacitor can smooth out the output signal much better than a low capacitor. that's way higher is more preferable & in stable wave forms.

(P.T.O)



Discussion:

In this experiment we learned about two types of rectifiers. Implementing how the rectifier works by using capacitor was really interesting. By simulating the half wave and full wave rectifier we saw how a capacitor can lower the ripple rate of signals in DC. The simulation part was a bit difficult to understand. But after some trial and error finally it worked as intended.


Akram Hossain Fahim
1812724042

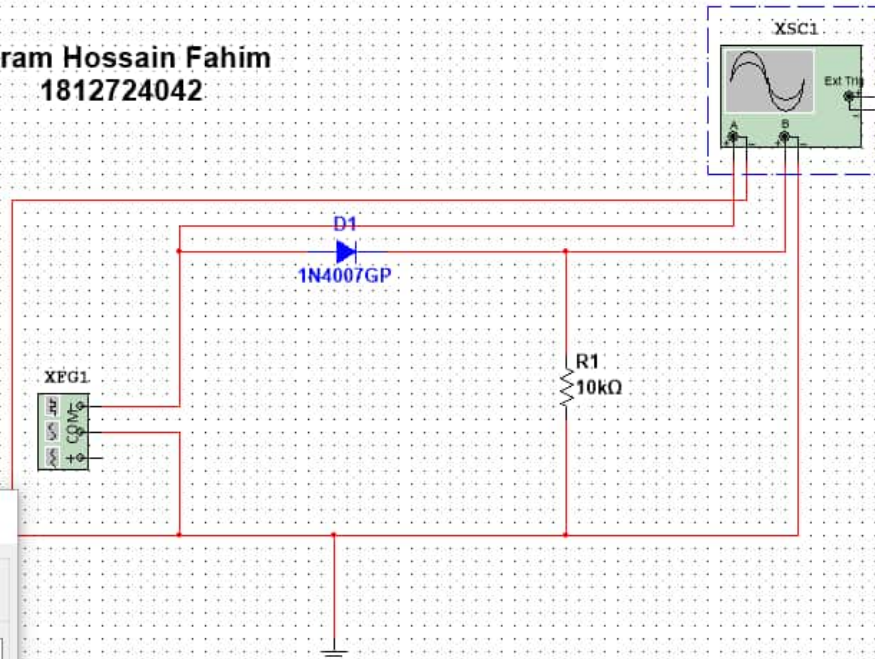

Oscilloscope-XSC1

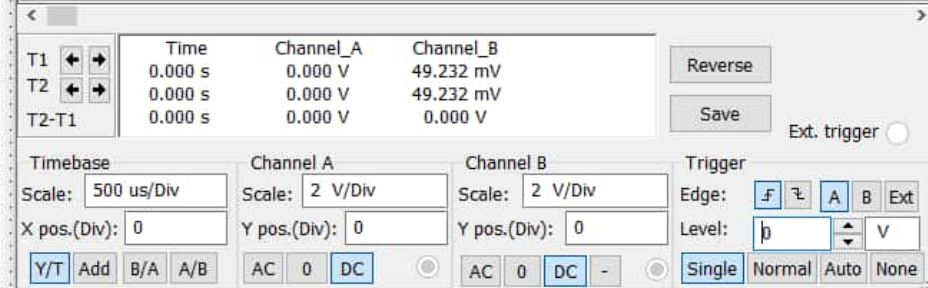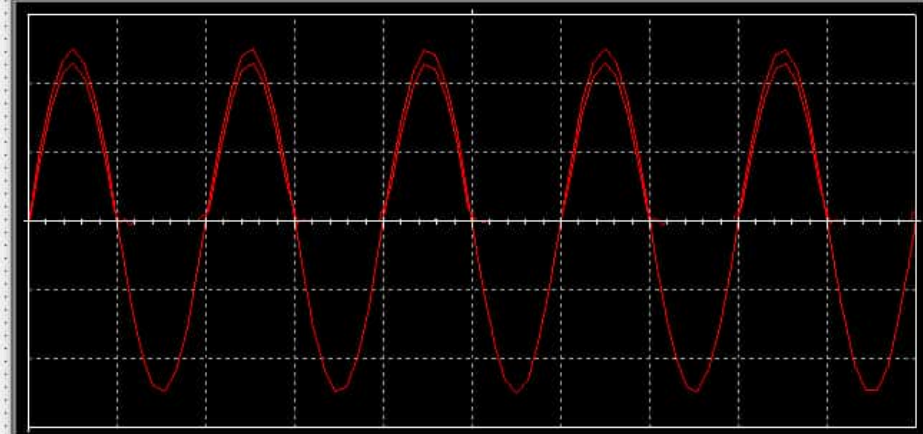

Akram Hossain Fahim
1812724042

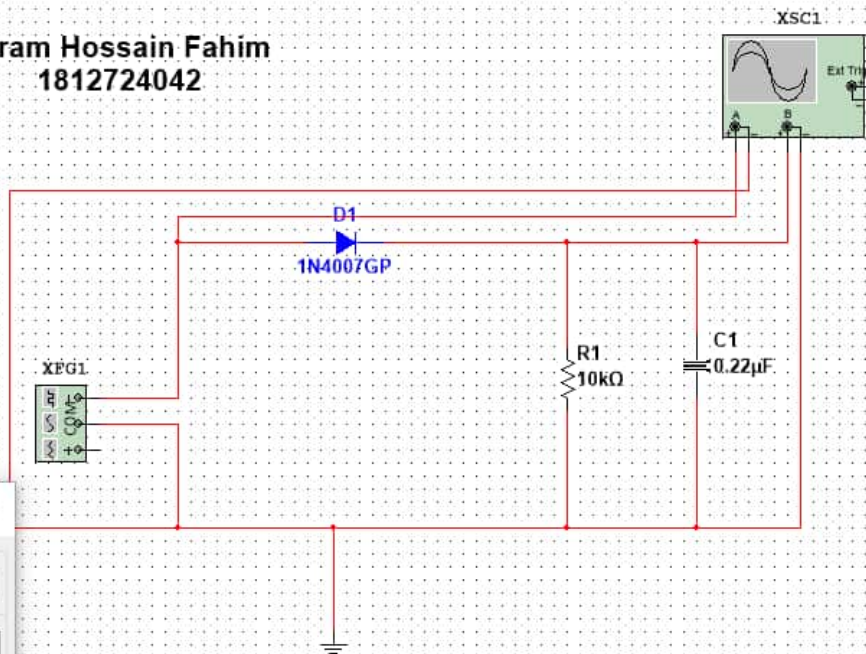

Function generator-XFG1

Waveforms


Signal options

Frequency:	1	kHz
Duty cycle:	50	%
Amplitude:	5	Vp
Offset:	0	V

Set rise/Fall time

Common

Oscilloscope-XSC1

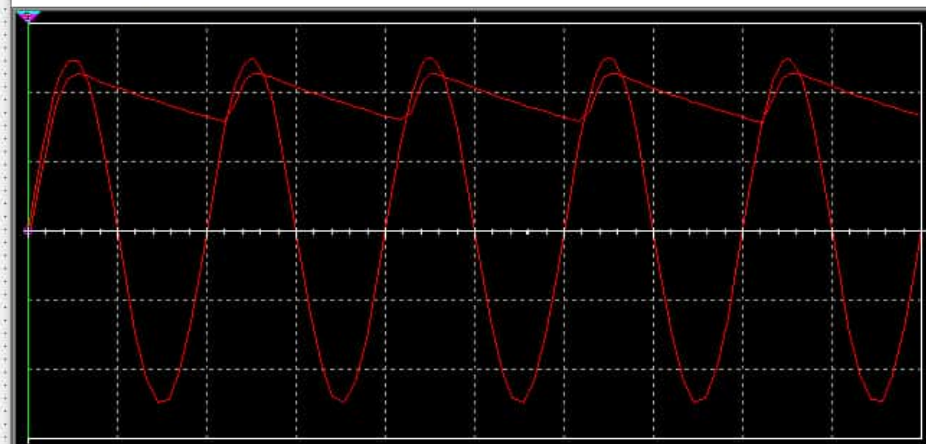

	Time	Channel_A	Channel_B
T1	0.000 s	0.000 V	84.924 mV
T2	0.000 s	0.000 V	84.924 mV
T2-T1	0.000 s	0.000 V	0.000 V

Reverse

Save

Ext. trigger

Timebase

Scale: 500 us/Div

Channel A

Scale: 2 V/Div

Channel B

Scale: 2 V/Div

Trigger


Edge: F, A, B, Ext

Level: 0 V


Single Normal Auto None

Y/T Add B/A A/B AC 0 DC -

Akram Hossain Fahim
1812724042

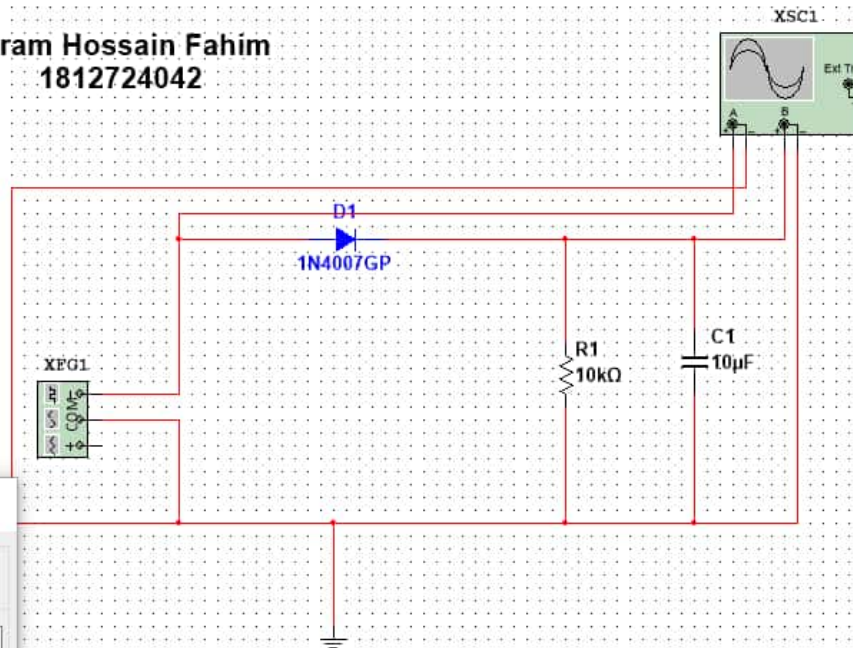


Oscilloscope-XSC1


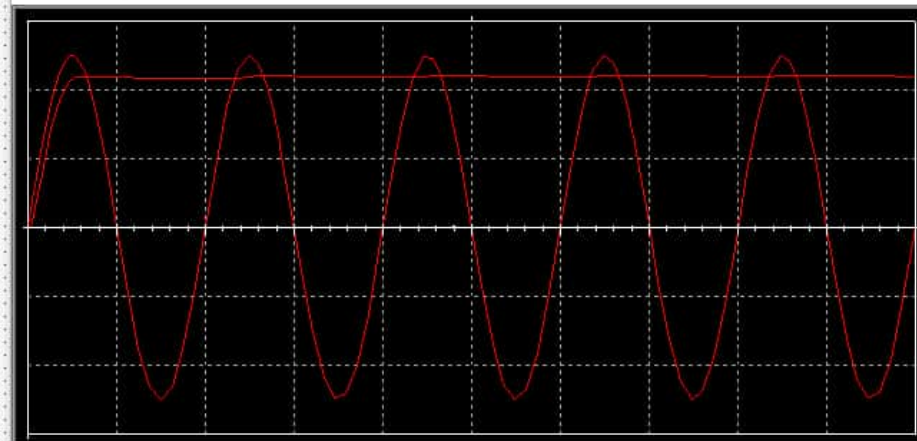


	Time	Channel_A	Channel_B	
T1	0.000 s	0.000 V	10.185 mV	Reverse Save Ext. trigger <input type="radio"/>
T2	0.000 s	0.000 V	10.185 mV	
T2-T1	0.000 s	0.000 V	0.000 V	
Timebase		Channel A	Channel B	Trigger
Scale:	500 us/Div	Scale: 2 V/Div	Scale: 2 V/Div	Edge: <input type="radio"/> F <input type="radio"/> ∇ <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> Ext
X pos.(Div):	0	Y pos.(Div): 0	Y pos.(Div): 0	Level: 0 V
<input checked="" type="radio"/> Y/T <input type="radio"/> Add <input type="radio"/> B/A <input type="radio"/> A/B	<input type="radio"/> AC <input checked="" type="radio"/> 0 <input type="radio"/> DC	<input type="radio"/> AC <input checked="" type="radio"/> 0 <input type="radio"/> DC	<input type="radio"/> - <input checked="" type="radio"/>	<input checked="" type="radio"/> Single <input type="radio"/> Normal <input type="radio"/> Auto <input type="radio"/> None


Akram Hossain Fahim
1812724042

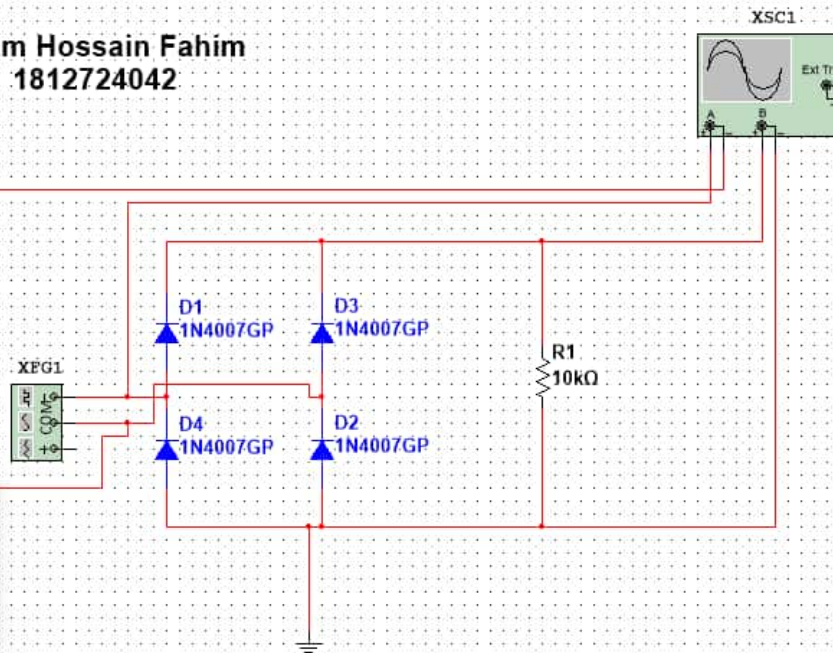



Oscilloscope-XSC1

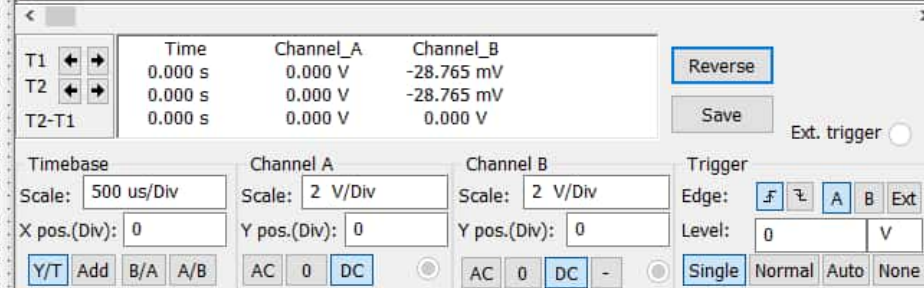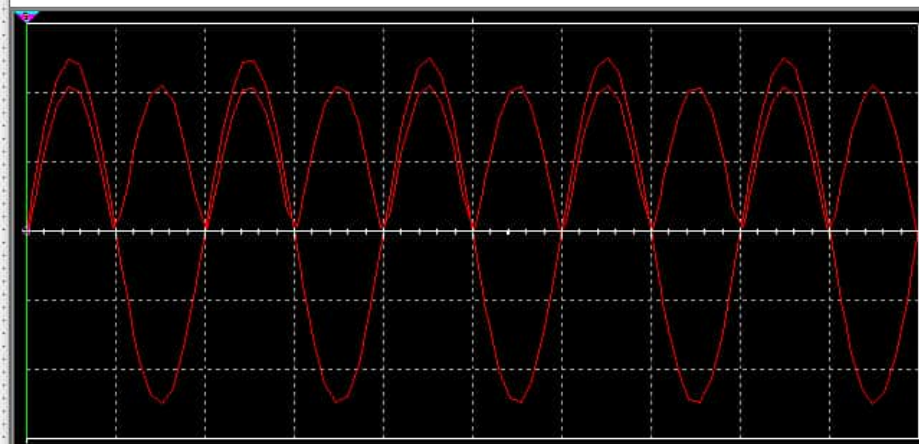


Akram Hossain Fahim
1812724042

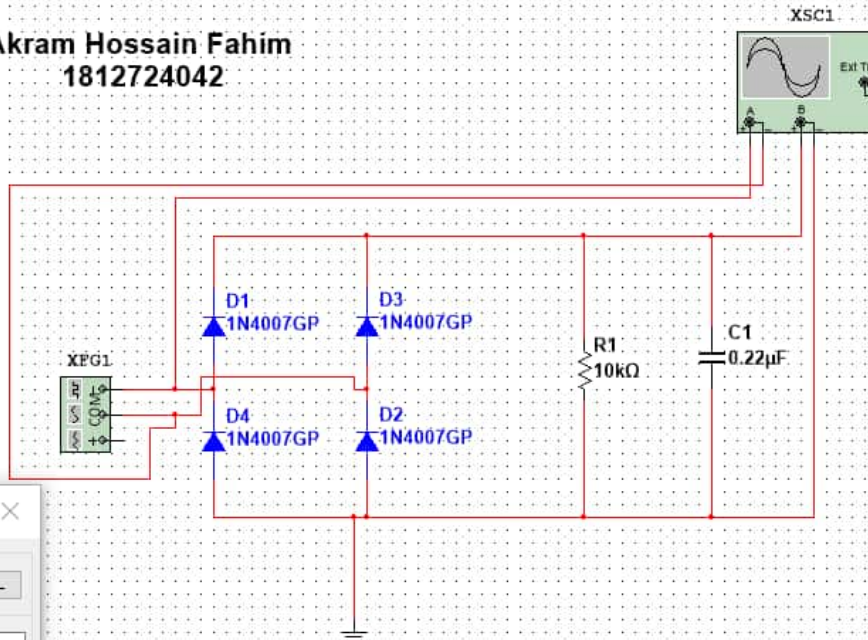

Oscilloscope-XSC1

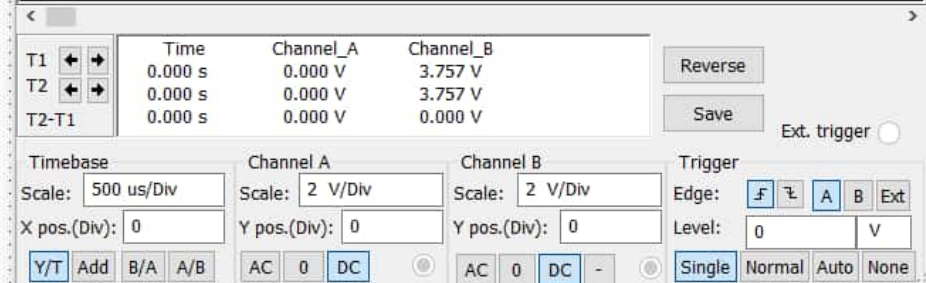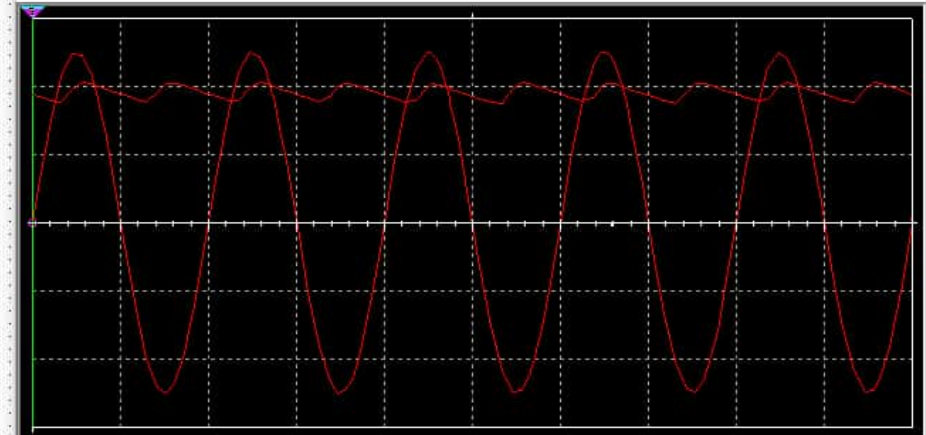

Akram Hossain Fahim
1812724042

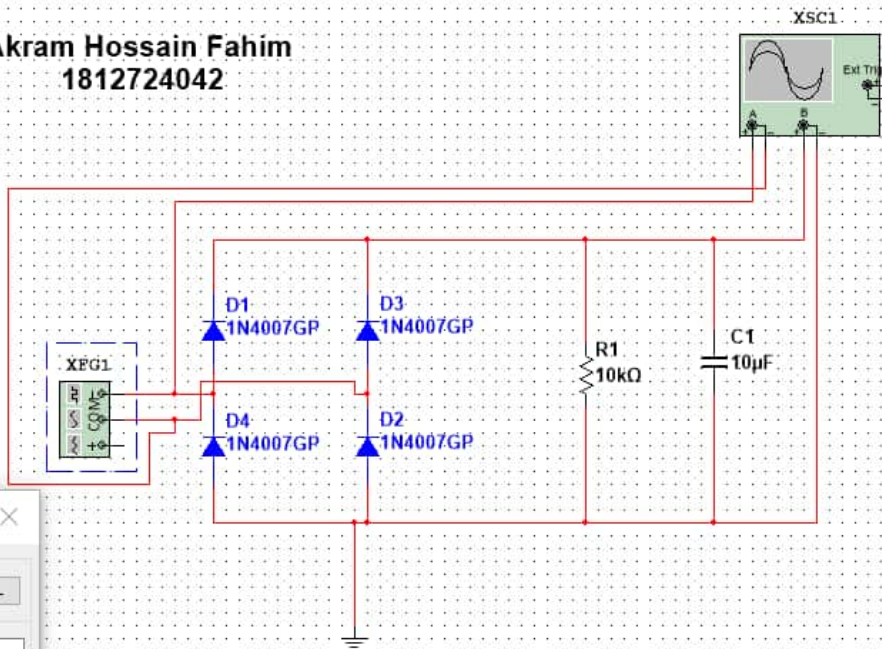

Oscilloscope-XSC1

