



North South University

Department of Electrical & Computer Engineering

LAB REPORT

Spring 2021

Course Code : EEE 111

Course Title: Analog Electronics - I

Section: 7

Experiment Number: 01

Experiment Name:

I-V Characteristics of diode

Experiment Date: 02 / 03 / 2021

Date of Submission: 16 / 03 / 2021

Course Instructor: Syeda Sarita Hassan

Submitted To: Fatema Zahra

LAB REPORT-01

Name of experiment: I-V Characteristics of diode

Objective:

The objective of this experiment is to study the I-V Characteristics of diode

Equipments and Components:

| Serial no. | Component Details | Specification | Quantity |
|------------|--------------------|---------------|-------------|
| 1 | P-n junction diode | 1N4007 | 1 piece |
| 2 | Resistor | 1 k Ω | 1 piece |
| 3 | DC power supply | | 1 unit |
| 4 | Signal generator | | 1 unit |
| 5 | Trainer Board | | 1 unit |
| 6 | Oscilloscope | | 1 unit |
| 7 | Digital Multimeter | | 1 unit |
| 8 | Chords and wire | | as required |

Theory:

A diode is a bi-polar (one end is positive and another is negative). A diode can be in two states depending on the direction of power. If a diode's positive end is connected to a power supply's positive end then it will be in Forward biasing and behave as a short circuit. And if the diode's positive end is connected to the power supply's negative end then it'll be in reverse biasing and behave as an open circuit.

Circuit Diagram:

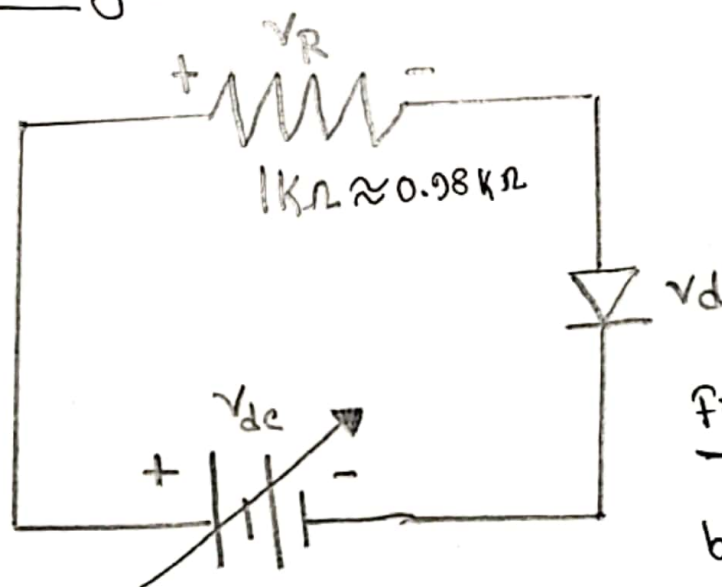


Fig: Circuit Diagram of a Forward biasing diode


Data Table :

| $V_{de} (V)$ | $V_d (V)$ | $V_R (V)$ | $I_d = V_R/R$ (mA) |
|--------------|-----------|-----------|-----------------------|
| 0 | 0 | 0 | 0 |
| 1 | 0.42 | 0.57 | 0.58 |
| 2 | 0.48 | 1.51 | 1.54 |
| 4 | 0.53 | 3.46 | 3.53 |
| 6 | 0.56 | 5.43 | 5.54 |
| 8 | 0.58 | 7.41 | 7.56 |
| 10 | 0.59 | 9.40 | 9.59 |
| 12 | 0.60 | 11.39 | 11.62 |
| 14 | 0.61 | 13.38 | 13.65 |
| 16 | 0.62 | 15.37 | 15.68 |

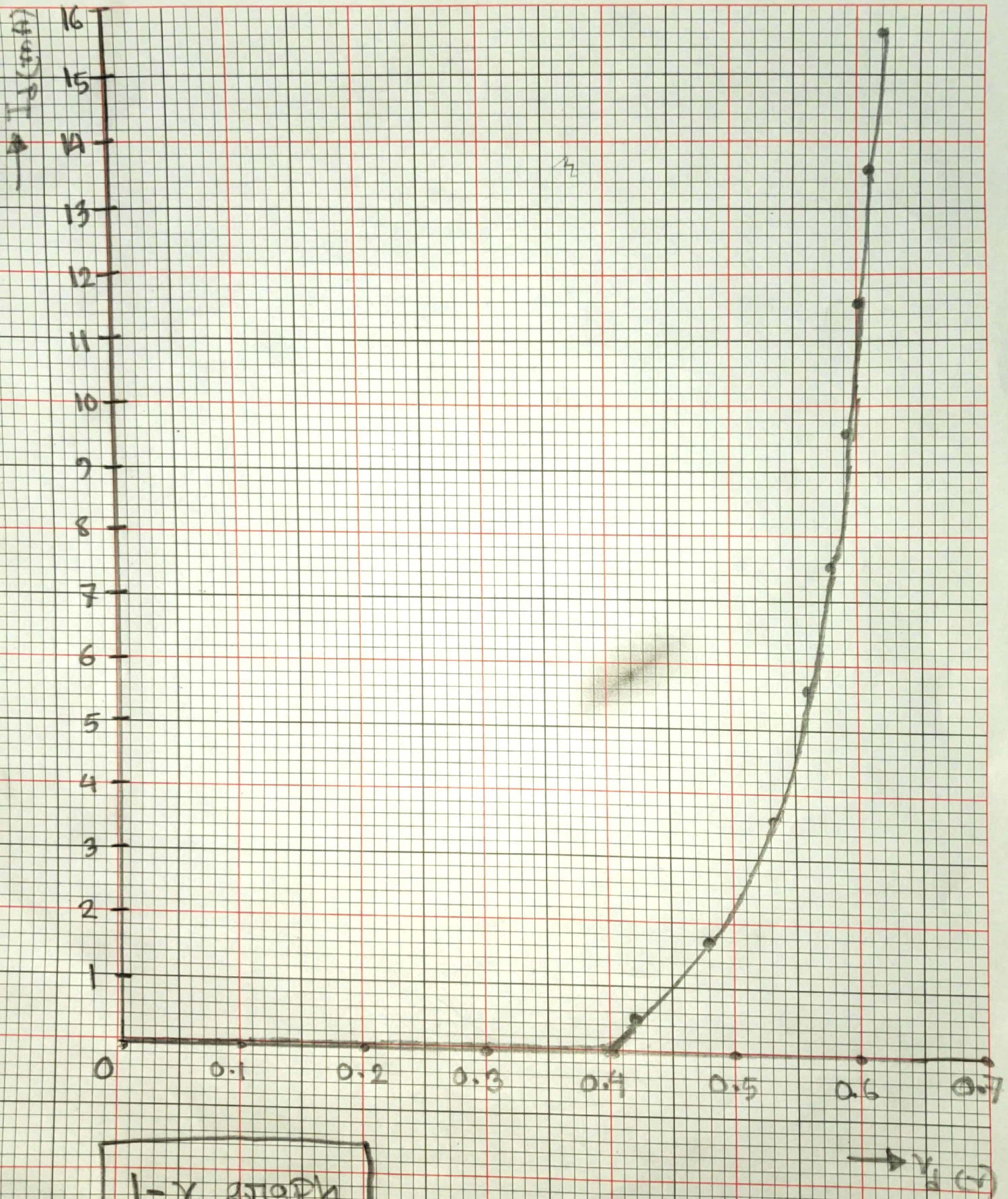Questions:

① Draw the I-V characteristics curve of diode from the reading obtain in this experiment.

Ans: The graph of the curve has been attached with the lab report.



② Calculate the static resistance for $I_d = 5\text{mA}$ and $I_d = 10\text{mA}$.

Ans:

we know,

$$R_d = \frac{V_d}{I_d}$$

for $I_d = 5\text{mA}$, V_d is 0.55V . (from graph)

$$\begin{aligned}\therefore R_d &= \frac{0.55\text{V}}{5\text{mA}} \\ &= 110\Omega\end{aligned}$$

for $I_d = 10\text{mA}$, V_d is 0.595V (from graph)

$$\begin{aligned}\therefore R_d &= \frac{0.595\text{V}}{10\text{mA}} \\ &= 59.5\Omega\end{aligned}$$

③ Determine the Q-point for the circuit in Figure -6, when $V_{dc} = 8$ volt.

Ans:

From the data table we can see for 8 volt V_{dc} , V_d is 0.58 volts and I_d is 7.56 mA.


So the Q-point is (0.58, 7.56)

~~A~~

Discussion:

In this experiment we learned about how a diode functions depending on the direction of power. We have experimented with a forward biasing circuit to learn about the threshold voltage of the diode. Which in this case was between 0.6V-0.7V. We have also simulated the circuit in Multisim.

Lab - 01

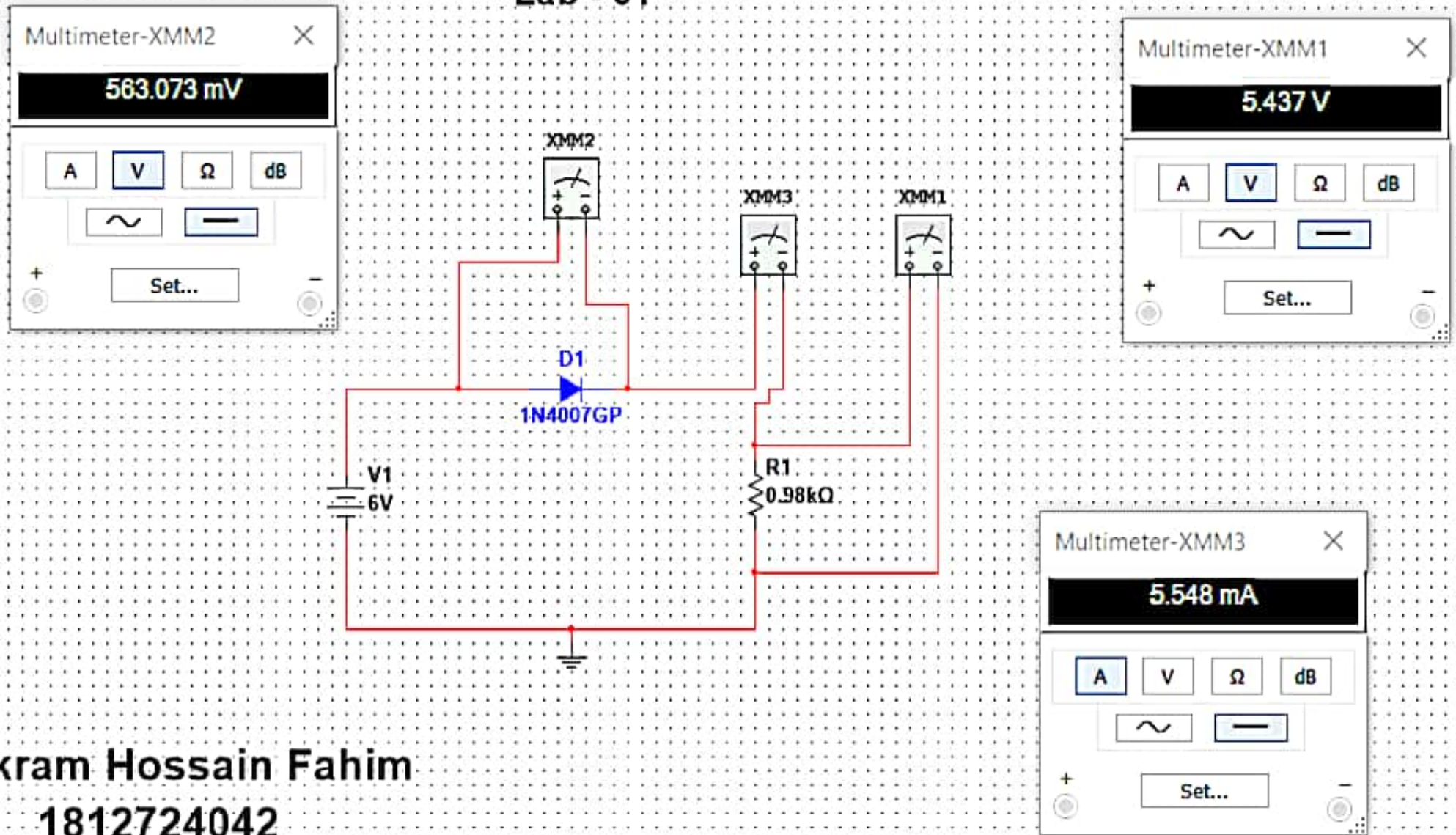

Akram Hossain Fahim
1812724042