



North South University
Department of Electrical & Computer Engineering

LAB REPORT
Spring 2021

Course Code : EEE 111

Course Title: Analog Electronics - I

Section: 7

Experiment Number: 06

Experiment Name:

The BJT Biasing Circuits

Experiment Date: 20 / 04 / 2021

Date of Submission: 29 / 04 / 2021

Course Instructor: Syeda Sarita Hassan

Submitted To: Fatema Zahra

Name of experiment:

The BJT Biasing Circuits

Objective:

Study of the BJT Biasing Circuits.

Equipments and Components:

- 1) Npn transistors — C828, BD135 — 1 piece each
- 2) Resistor — 470Ω , 560Ω , $220k\Omega$ — 1 piece each
- 3) POT — $10k\Omega$ — 1 unit.
- 4) Trainer Board — 1 unit.
- 5) DC power supply — 1 unit.
- 6) Digital Multimeter — 1 unit.
- 7) Chords and wire — as required.

(P.T.O)

Theory:

Biassing a BJT circuit intends to give fitting direct possibilities and flows utilizing on outside resources, To build up an operating point or Q-point in the active ~~region~~ region. When the Q-point is established, the input signal should cause an output signal to same waveform. So we can say the main objective of biassing a BJT circuit is to choose the proper Q-point for faithful reproduction of the input signal. We will work with Fixed bias circuit and Self bias circuit.

(P.T.O)

Circuit Diagrams:

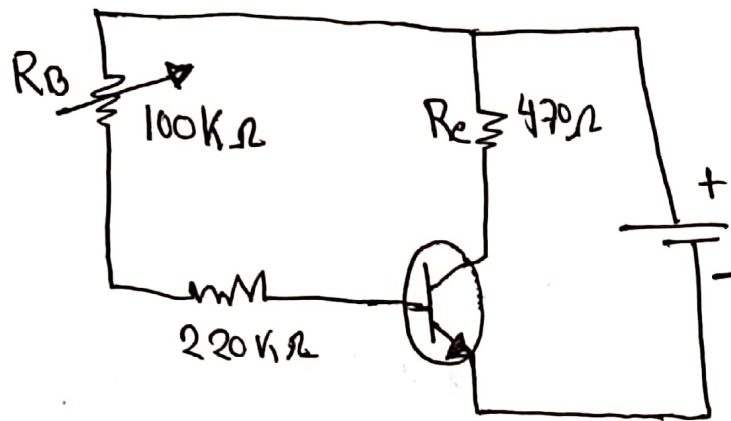


Fig- Fixed Bias Circuit.

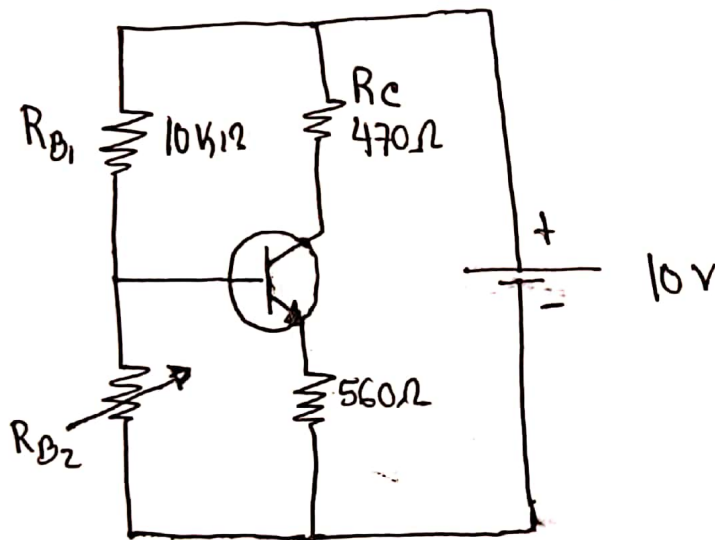


Fig- Self Bias Circuit.

Tables:

Data For Fixed Bias Circuit -

Transistor	R_e (Ω)	V_e (Volt)	$I_e = V_e / R_e$ (Amp)	V_{CE} (Volt)	Q-point
C828	470	11.00	23.4	11.00	(11, 23.4)
BD135	470	17.02	10.21	17.02	(17.02, 10.21)

Data For self Bias Circuit -

Transistor	R_e (Ω)	V_e (Volt)	$I_e = V_e / R_e$ (Amp)	V_{CE} (Volt)	Q-point
C828	470	16.75	11.18	10.46	(16.75, 11.18)
BD135	470	17.01	10.6	11.00	(17.01, 10.6)

Question And Answer:

① Ans:

Self bias circuit shows better stability. The variation of the Q point is very little so the change in input and output waveform is very little compared to fixed bias circuit. So the self bias circuit is more stability.

②Ans:


The graph is attached with the Report.

Discussion:

In this experiment we have learned about how the biasing in BJT circuit affects its stability. we have used fixed bias circuit and self bias circuit. The simulation was easy and i didn't face any difficulties.


Fixed bias circuit.

I_c (Amp)

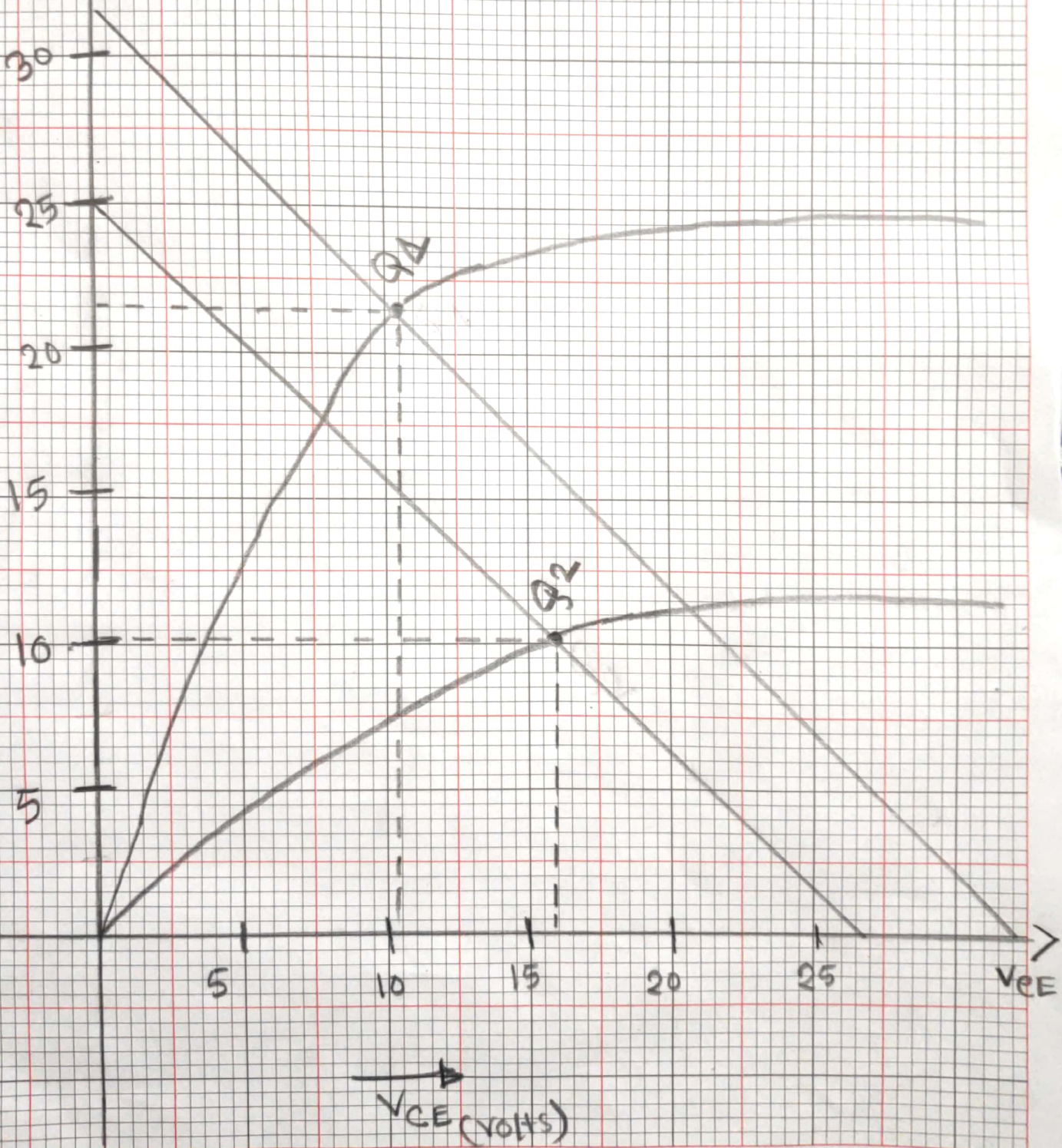


Abdham Hossain Fahim


Self bias circuit.

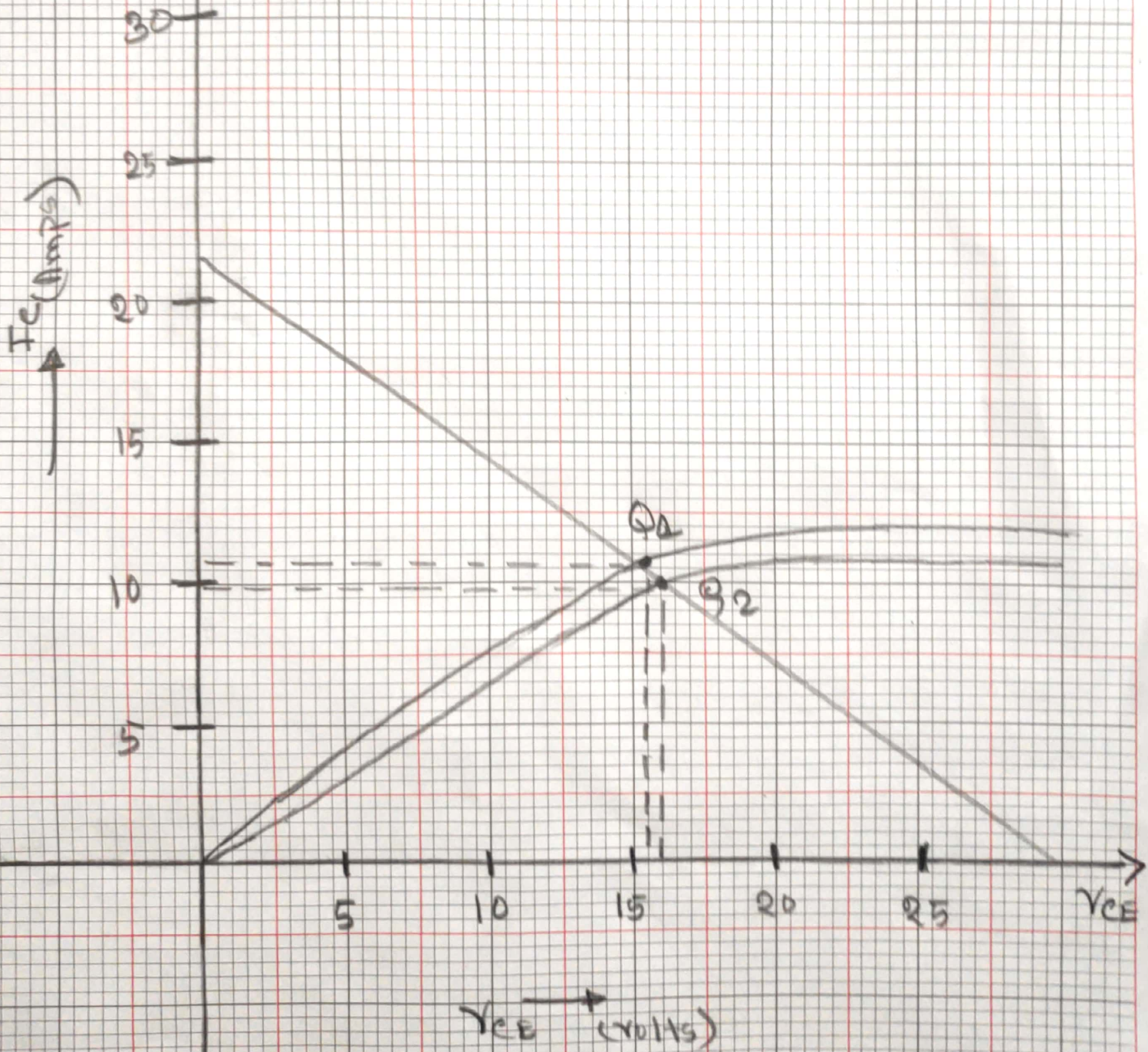

Akram Hossain Fahim
1812724042

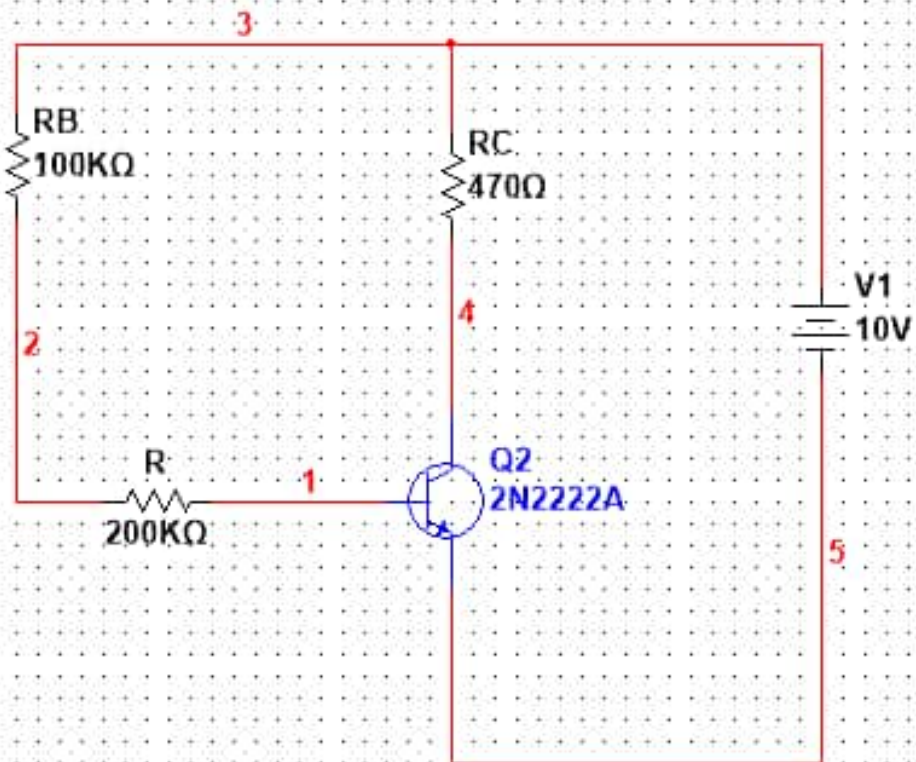

Fixed Bias Circuit

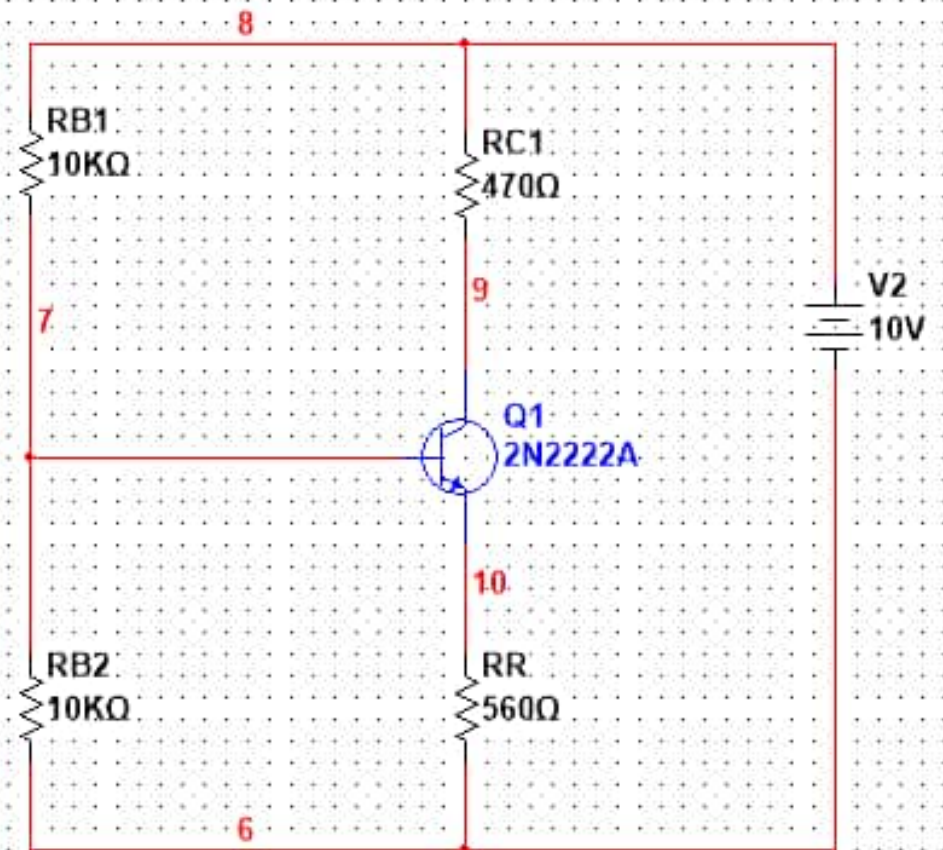

Self Bias Circuit