



North South University
Department of Electrical & Computer Engineering

LAB REPORT

Spring 2021

Course Code : EEE 111

Course Title: Analog Electronics - I

Section: 7

Experiment Number: 07

Experiment Name:

Study of Switching Characteristics

Experiment Date: 27 / 04 / 2021

Date of Submission: 03 / 05 / 2021

Course Instructor: Syeda Sarita Hassan

Submitted To: Fatema Zahra

Name of experiment:

Study of switching Characteristics

Objective:

Study all of the switching characteristics.

Equipments And Components:

- 1) MOSFET ——— IRF 540 ——— 1 piece each
- 2) Resistor ——— $1k\Omega$ ——— 1 piece each
- 3) POT ——— ——— 1 unit
- 4) Trainer Board ——— ——— 1 unit
- 5) DC Power Supply ——— ~~1 unit~~ 2 unit
- 6) Digital Multimeter ——— ——— 1 unit
- 7) Cords & wire ——— ——— as required

(P.T.O)

Theory:


MOSFET (Metal Oxide Semiconductor Field Effect Transistors) belongs to the group of insulated gate field effect transistor. MOSFET has three terminal gate (G), source (S) and drain (D).

There are two types of MOSFET

- i) DE-MOSFET
- ii) EN-MOSFET

A common application of MOSFET is switching in analog and digital circuits.

Circuit Diagram:

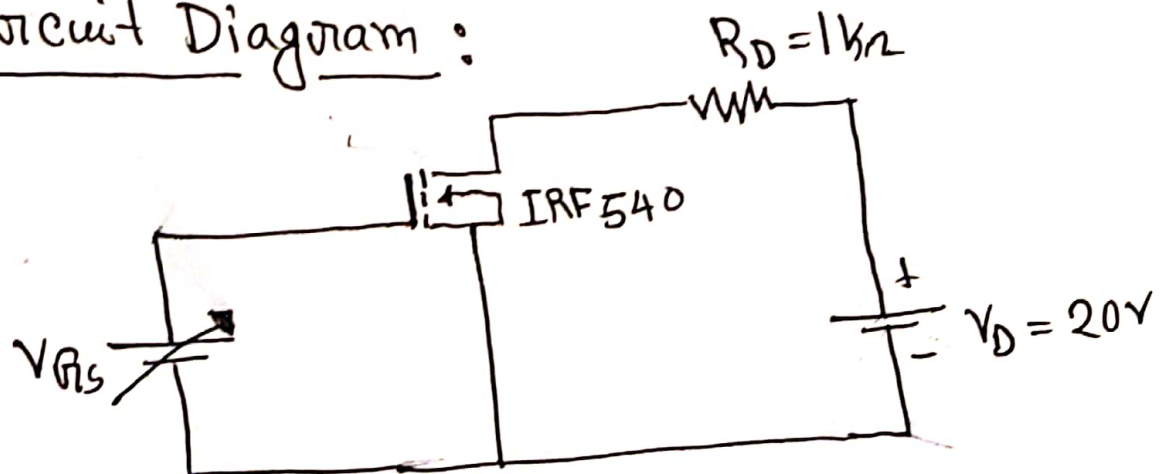

tables:

$V_{DD} = \text{20V}$				$V_{DD} = \text{15V}$			
V_{GS}	V_{DS}	V_L	I_D	V_{GS}	V_{DS}	V_L	I_D
0V	20V	-20.13 μ V	20.6nA	0V	15V	-15.1 μ V	15.27nA
0.5V	20V	-20.131 μ V	20.606nA	0.5	15V	-15.1 μ V	15.27nA
1V	20V	-20.132 μ V	20.606nA	1V	15V	-15.1 μ V	15.27nA
2.5V	7.145V	-12.85V	12.58mA	2.5	2.41V	-12.58V	12.58mA
3V	0.24V	-19.75V	19.75mA	3V	0.17V	-14.82V	14.82mA
4V	0.12V	-19.87V	19.87mA	4V	0.09V	-14.93V	14.93mA
5V	0.09V	-19.90V	19.90mA	5V	0.06V	-14.93V	14.93mA

Answer & Question:

① Ans: The simulation has been attached to the lab report.

Discussion:

In the experiment we have learned about the switching characteristics of MOSFET. We learned how increasing the gate voltage affects the circuit. The multisim simulation was easy. I didn't face any major difficulty.

Akram Hossain Fahim
1812724042

