#### 11. Simulation:


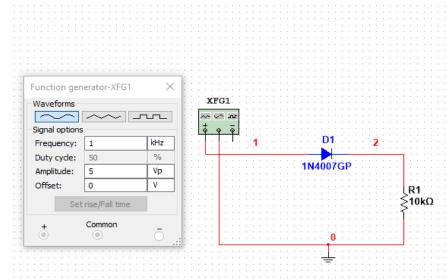


Figure: Half Wave Rectifier

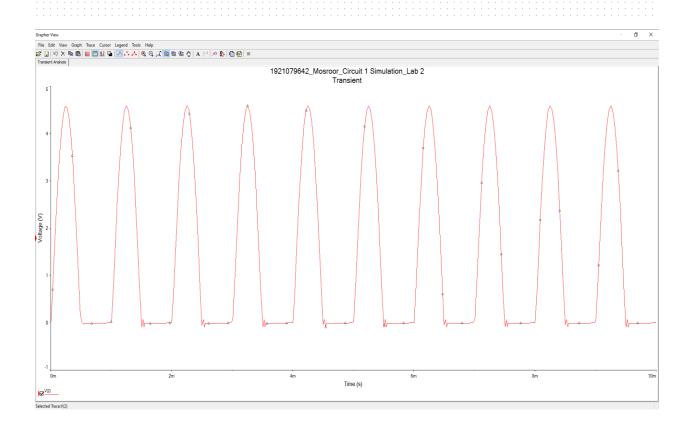


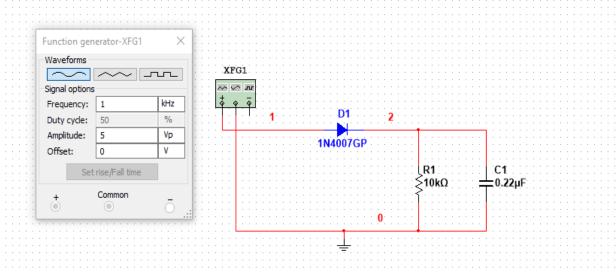


Figure: Half Wave Rectifier using 0.22 µF Capacitor

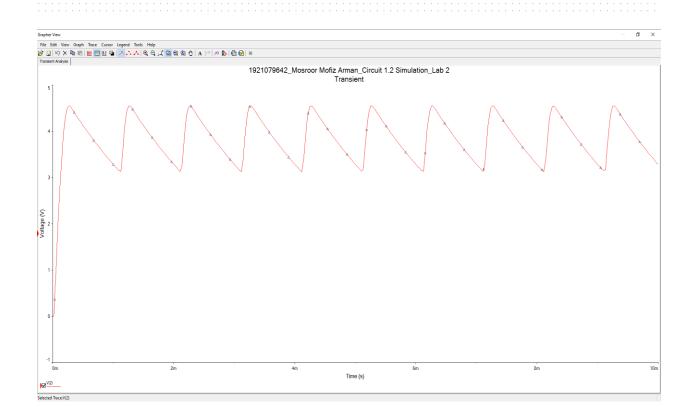


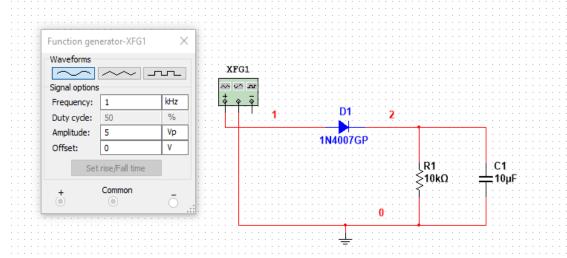


Figure: Half Wave Rectifier using 10 µF Capacitor

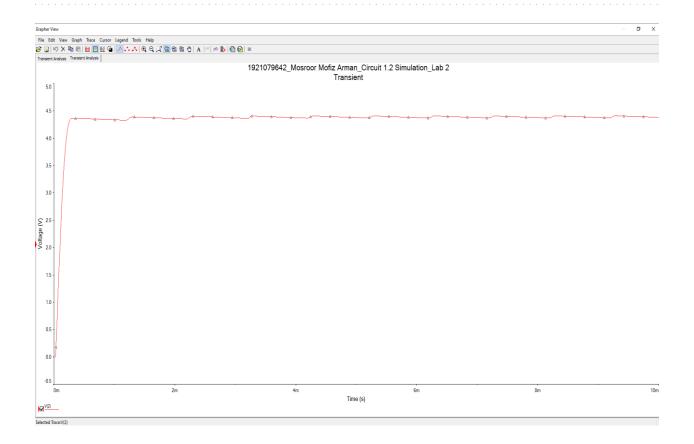


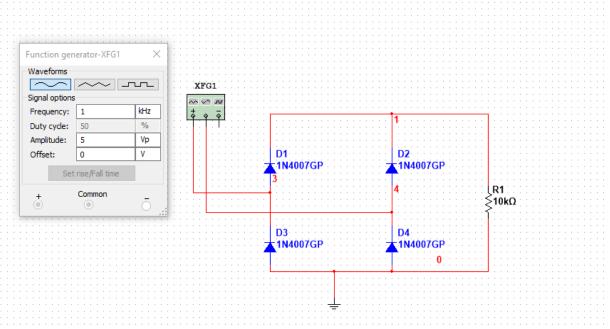


Figure: Full Wave Rectifier

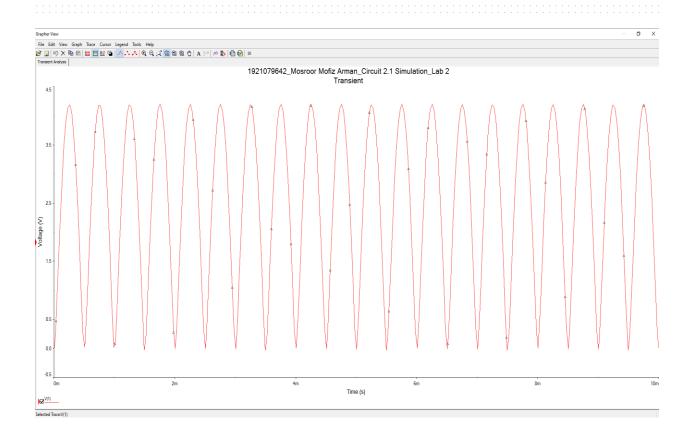


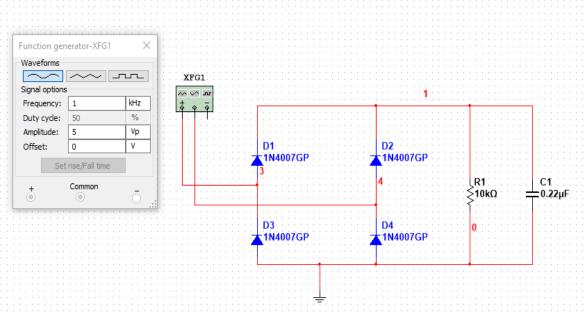


Figure: Full Wave Rectifier using 0.22 µF Capacitor

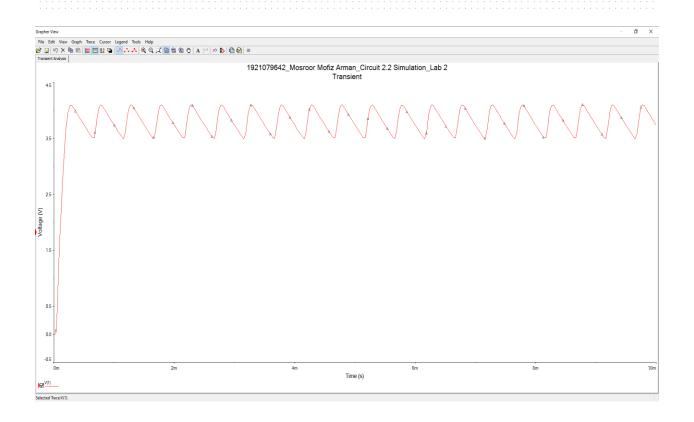

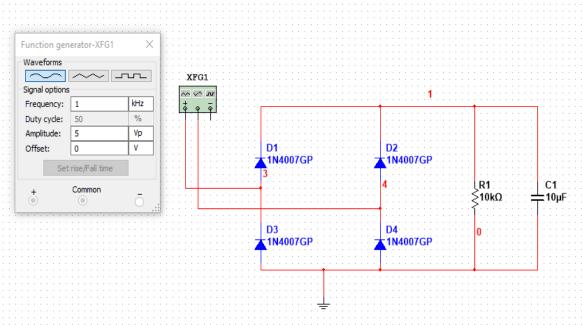


Figure: Full Wave Rectifier using 10 µF Capacitor

